
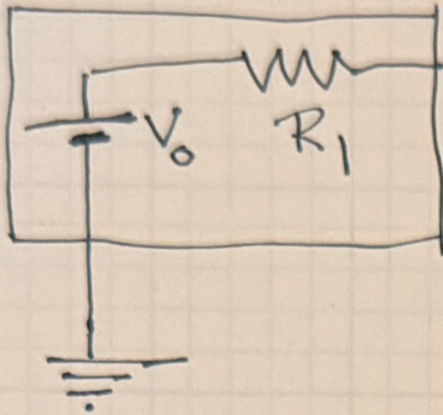


Device 1

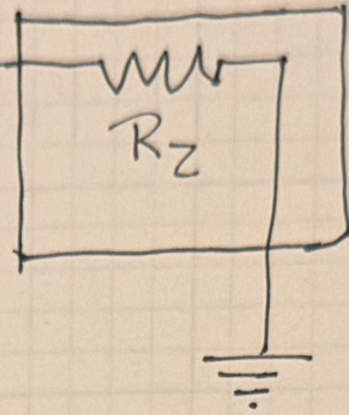

Device 2



For what value of R_2 does Device 2 use the most power?

Use $V_0 = 12\text{V}$ and $R_1 = 3\Omega$.

